Title: Implement full adder using VHDL.